



Technological Institute of the Philippines
College of Computer Studies
S.Y. 2025 - 2026

Mangahas, King Angelo B.	April 2, 2025
CITE 006 - IT32S3	Mr. Alfio Regla

11.1 | Traffic Light Simulation using Arduino and Tinkercad

Traffic Light Simulation using Arduino and Tinkercad

Lesson Objectives:

1. Connect and simulate a circuit using three LEDs (Red, Yellow, Green) and resistors.
2. Write an Arduino program to control the LEDs in a traffic light sequence.
3. Use Tinkercad to test and debug the circuit and code.

Intended Learning Outcomes (ILOs)

By the end of this activity, students should be able to:

1. Understand and apply circuit design using a breadboard and Arduino.
2. Demonstrate proper use of LEDs, resistors, and digital pins in an Arduino circuit.
3. Write and upload Arduino code to control LEDs with timing delays.
4. Simulate a traffic light system in Tinkercad.
5. Analyze and debug wiring or coding errors in the circuit.

Circuit Design in Tinkercad

Required Components:

- 1 Arduino Uno
- 3 LEDs (Red, Yellow, Green)
- 3 Resistors (220Ω each)
- 1 Breadboard
- Connecting Wires




Technological Institute of the Philippines
College of Computer Studies
S.Y. 2025 - 2026

Component List

Name	Quantity	Component
U1	1	Arduino Uno R3
D1	1	Red LED
D2	1	Green LED
D3	1	Yellow LED
R1 R2 R3	3	220 kΩ Resistor

Connections:

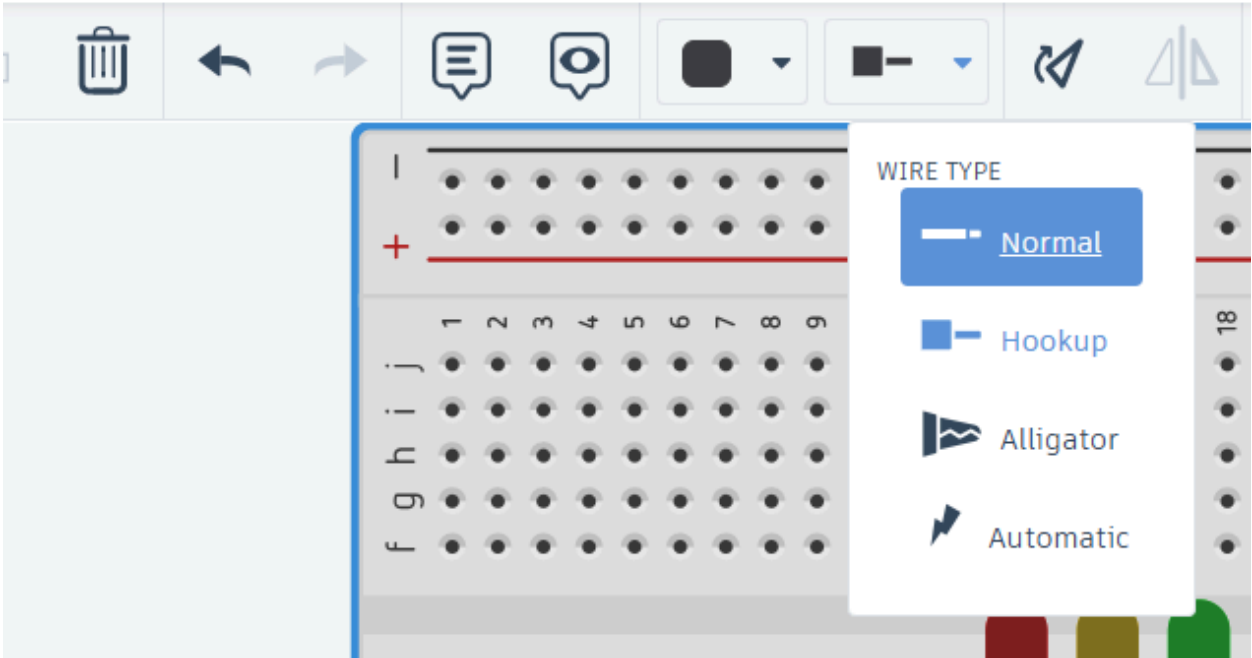1. Connect each **LED’s positive leg** to Arduino **pins 8, 9, and 10** respectively, using **220Ω resistors**.
2. Connect each **negative leg** of the LEDs to the **GND rail** on the breadboard.
3. Use a **jumper wire** to connect the **GND rail** to the **GND pin** of the Arduino.
4. Verify all connections before proceeding.




- **Hookup Wires (Recommended)** – These work like jumper wires on a breadboard.
- **Normal Wires** – These can also be used, but they don’t automatically snap between breadboard rows.
- **Alligator Clips** – Not needed for breadboards; use only for external components.




Technological Institute of the Philippines
College of Computer Studies
S.Y. 2025 - 2026

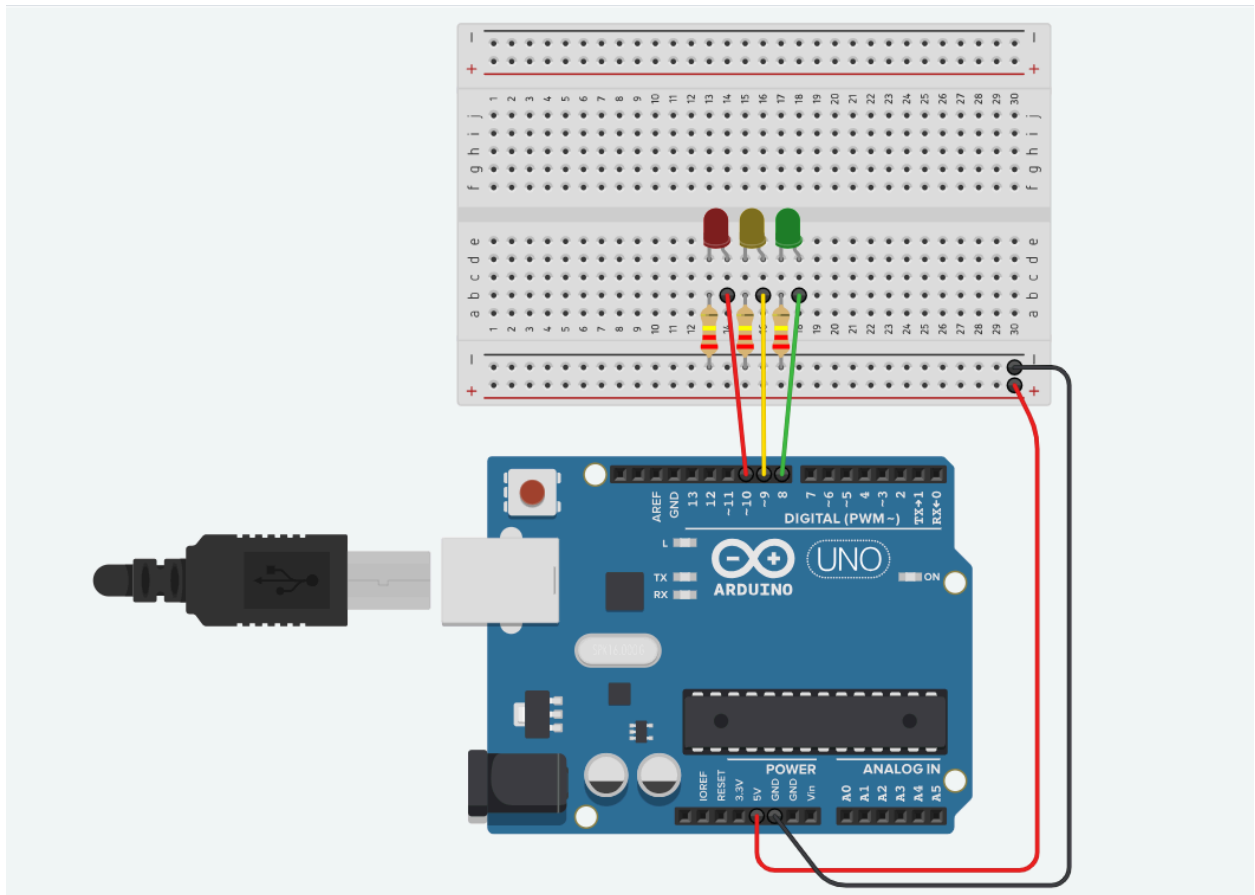- **Automatic Wires** – These adjust to connections but may not always follow the expected paths.



4. Arduino Code


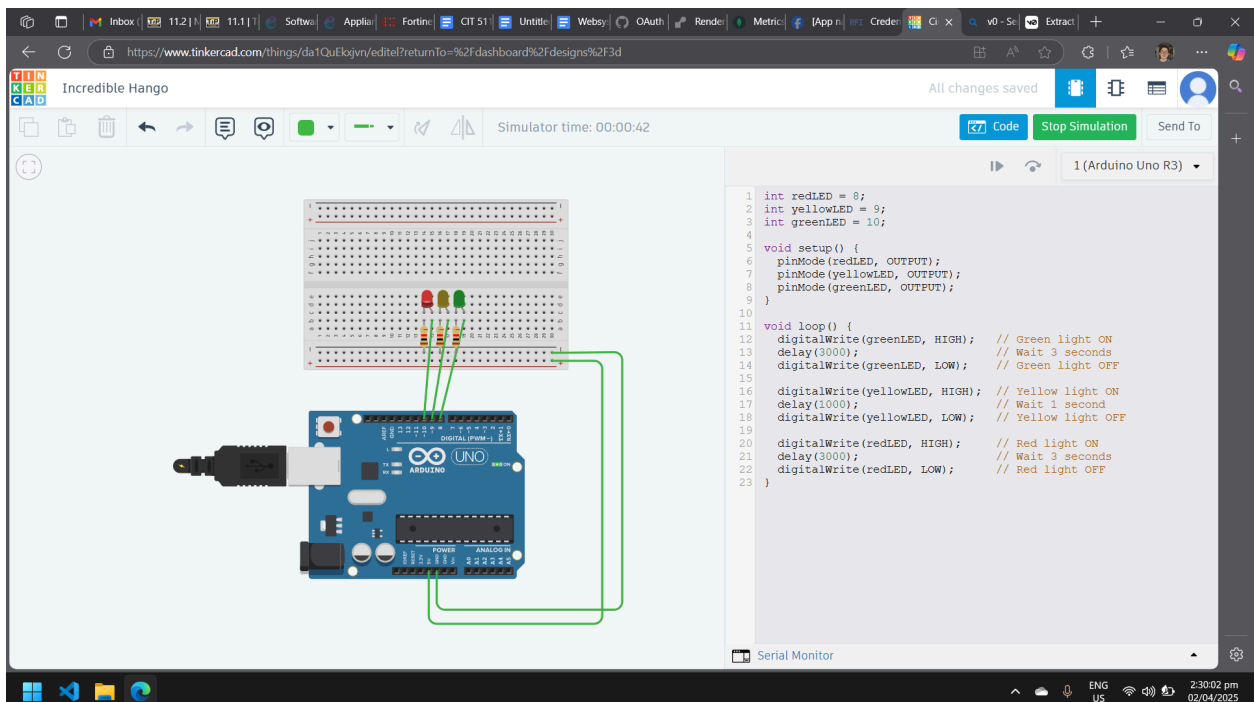




Technological Institute of the Philippines
College of Computer Studies
S.Y. 2025 - 2026


Test the Setup

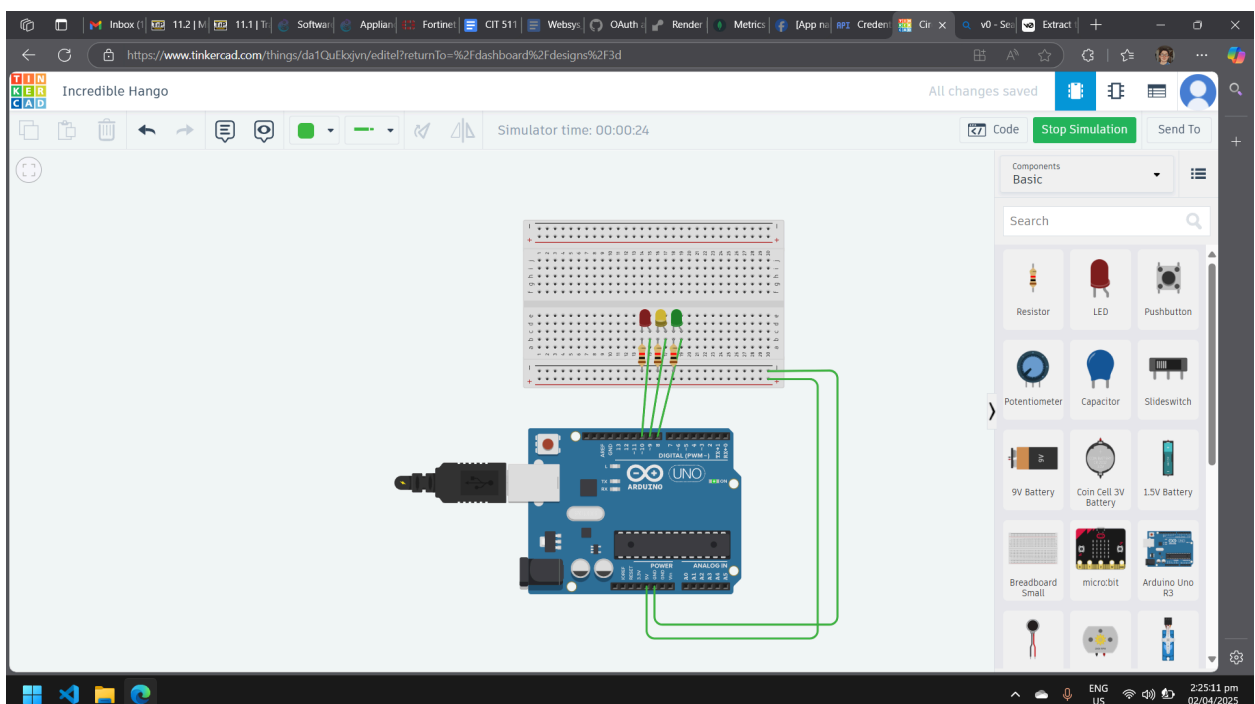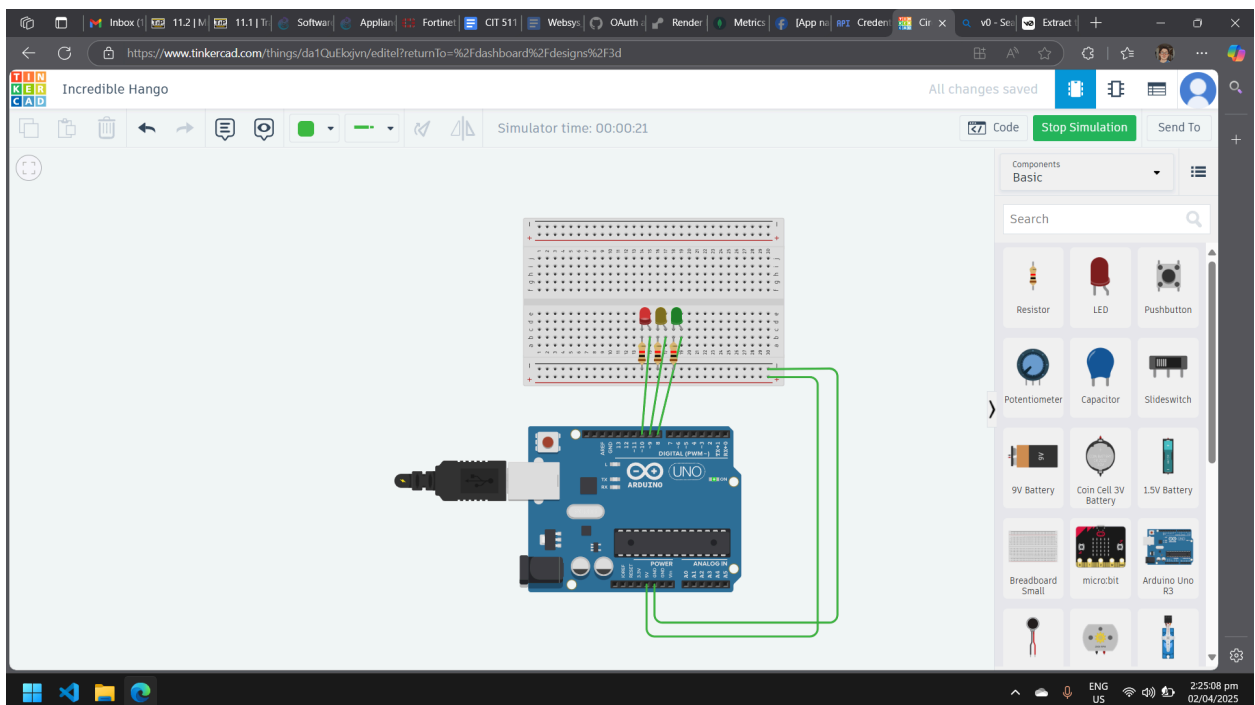- Run the Arduino code provided in your document.
- If the LEDs don't light up:
 - Check if you used **hookup wires** instead of the wrong type.
 - Verify that the **resistors are connected in series** (not in parallel).
 - Ensure that the **Arduino is powered (USB connected)**.





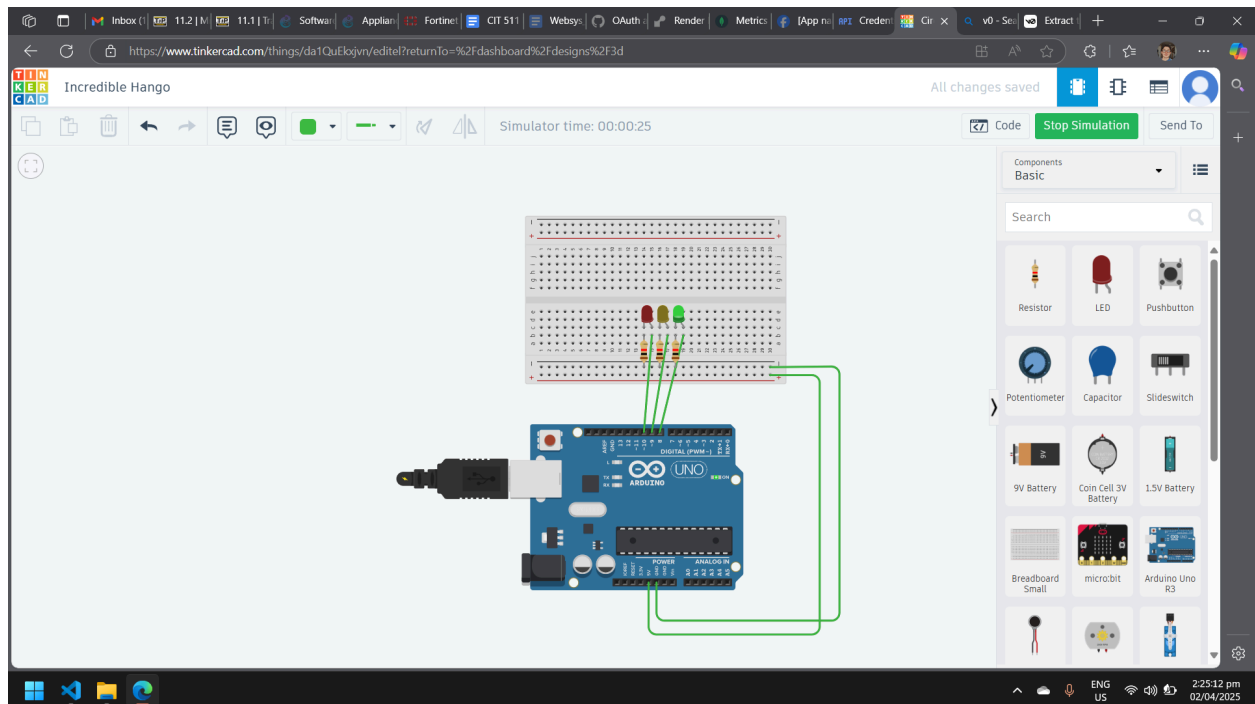Technological Institute of the Philippines
College of Computer Studies
S.Y. 2025 - 2026



5. Observations

[Describe if the simulation worked as expected.]

The Tinkercad simulation shows an Arduino Uno controlling three LEDs (red, yellow, and green) on a breadboard to create a traffic light system. The LEDs light up in sequence - green for 3 seconds, yellow for 1 second, and red for 3 seconds - repeating continuously. Each LED connects to the Arduino through a resistor using green wires, demonstrating a simple but practical application of microcontroller programming.

6. Problems Encountered & Solutions

[Describe any debugging or issues faced and how you solved them.]

The issue I encountered is using the tinkercad because it was my first time. I need to explore and ask for help to do the activity now.

7. Tinkercad Simulation Link

[Insert the link to your Tinkercad simulation.]

<https://www.tinkercad.com/things/da1QuEkxjyn/editel?returnTo=%2Fdashboard%2Fdesigns%2F3d&sharecode=1wvhFuMfNCpuVXs1yZhkH3w25NYr0AChiTZjoku5qUA>

8. Reflection

[What did you learn from this activity?]

What I have learned in today's activity is using the arduino. For now, this was easy because there's a guide for completing the task.